

EASTERN UNIVERSITY, SRI LANKA

FIRST EXAMINATION IN SCIENCE - 2009/2010

FIRST SEMESTER (PROPER/REPEAT)

(July/August 2011)

PH 202 ELECTRONICS I



Time: 01 hour.

Answer ALL Questions

1. What do you mean by intrinsic semiconductor?


Explain how an intrinsic semiconductor, for example pure silicon, may be converted into

(a) N - type semiconductor

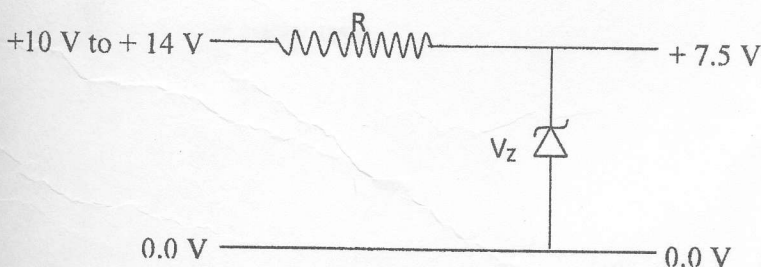(b) P - type semiconductor

Discuss the terms Junction break down, Zener break down and Avalanche break down.

The figure shows regulated voltage supply circuit. The input voltage varies from 10 V to 14 V. The required output voltage is 7.5 V.





- i. Name the type of diode required in this circuit.
- ii. What voltage rating should be chosen for the diode?
- iii. In which bias direction is the diode connected?

- iv. If the minimum diode current is 10 mA and the required output current from the circuit is 100 mA , Calculate;
- The current through the resistance R , when the output current is 100 mA
 - The voltage across the resistor R , when the input voltage is at minimum of 10 V .
- v. The input voltage now rises to its maximum of 14 V . Calculate;
- the voltage across R ,
 - the current through R at this voltage
 - the power dissipated by R at this voltage
- vi. The power supply input voltage remains at 14 V , but no current is drawn from the output of the regulator circuit. Find;
- the current through the diode
 - the power dissipated by the diode



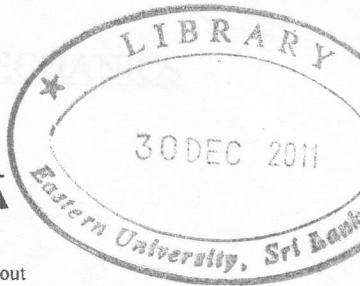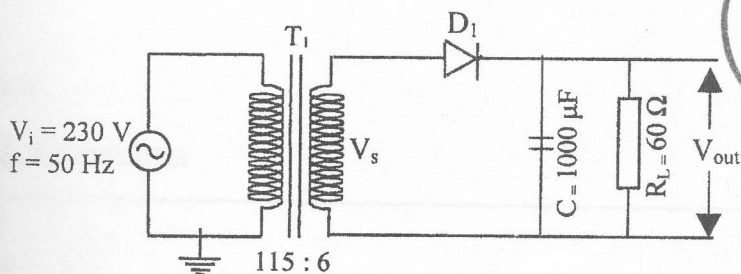2. Explain using circuit diagram function of a half wave rectifier, and indicate the direction of flow of current for any cycle of a.c. voltage. Hence derive an expression for mean output current I_{dc} .

Consider the half wave rectifier circuit given below.



- (i) Find the secondary voltage V_s
- (ii) The average value of current I_{dc}
- (iii) Average dc voltage across R_L
- (iv) r.m.s value of current I_{rms}
- (v) r.m.s voltage across R_L
- (vi) Ripple factor
- (vii) Peak inverse voltage

Prove any formula you may use.