



2

Time: 01 hour.

Answer ALL Questions

1. A pure resistor and an inductor are connected in series to a battery of e.m.f. E as shown in figure 1.

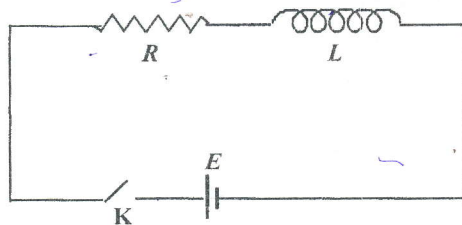


Figure 1

$\frac{dI}{dt} = \frac{E}{L} - \frac{R}{L}I$

When the key K is closed, the current I start to increase. If the inductor (L) was not present, the current would rise rapidly to a maximum steady value $I_0 = \frac{E}{R}$.

According to Faraday's and Lenz's law a self-induced electromotive force $L \frac{dI}{dt}$ appears due to the inductance L which opposes the rise of the current. Show that immediately after key K is closed, the current in the circuit at time (t) is given by

$$I = I_0 \left[1 - \exp\left(-\frac{R}{L}t\right) \right].$$

A relay, having an inductance 5.0 H and resistance 200Ω operates with a current 1.5 mA . When the relay is switched to a dc voltage of 0.5 V ,

- (a) how long will the relay take to operate?
 - (b) what will be the rate of increase of current at the instant of operation?
2. If a sinusoidal alternating voltage signal having amplitude V_0 and angular frequency ω is represented by $V = V_0 \exp(j\omega t)$, then find the *complex impedance* of a pure resistor, capacitor and inductor when they are individually connected to the voltage $V = V_0 \exp(j\omega t)$.

A series LCR circuit is connected to an alternating voltage as shown in figure 2. Find expressions for the current through the circuit and the voltage across the inductor.

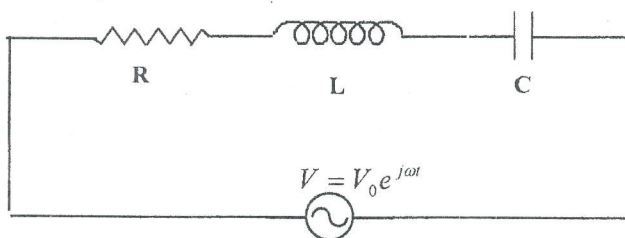


Figure 2

A coil having inductance of 460 mH and resistance of 48 Ω is connected in series with a capacitor having capacitance 9 μF and a r.m.s. voltage of 120 V is supplied to the circuit. What should be the frequency of the supplied voltage to obtain maximum current in the circuit? What is the voltage across the inductor under these conditions?