



EASTERN UNIVERSITY, SRI LANKA

THIRD EXAMINATION IN SCIENCE - 2009/2010

FIRST SEMESTER (RE-REPEAT)


(February/March 2013)

PH 301 ELECTRONICS II

Time: 01 hour.

Answer ALL Questions

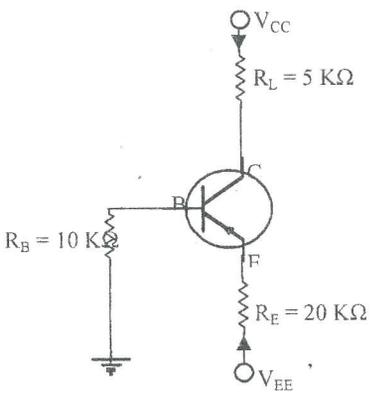- Describe the function of a bipolar junction transistor. Sketch and explain the input and output characteristics curves of a transistor.



In the above common emitter *n*p*n* transistor circuit, $R_B=10\text{ K}\Omega$, $R_L=05\text{ K}\Omega$, $R_E=20\text{ K}\Omega$, $V_{CC}=30\text{ V}$, $V_{EE}= -30\text{V}$ and common-emitter forward transfer ratio $\beta = 200$. Neglect the voltage drop between base and emitter terminals and find:

- Emitter current
- Base current
- Collector current
- Voltage drop between collector and emitter terminals.


- Briefly explain the characteristics of an ideal Operational Amplifier.

Why an open loop configuration of an op-amp is not suitable for linear applications?

Find the relationship between input and output voltages of the following Operational Amplifiers:

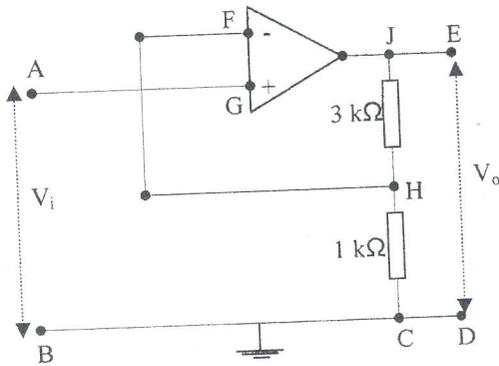- (a) Integrator
- (b) Adder
- (c) Differentiator

The figure shows an operational amplifier circuit using feedback.



- (a) Explain the advantages of using negative feedback in the circuit.
- (b) Using the letters on the circuit diagram, write the path of the negative feedback.
- (c) Write down the feedback factor β .
- (d) Op-amp in the diagram has a gain of 80,000, what will be the output voltage V_o when input voltage V_i is 0.2 V?