




EASTERN UNIVERSITY, SRI LANKA
DEPARTMENT OF MATHEMATICS
EXTERNAL DEGREE EXAMINATION IN SCIENCE – 2007/2008 & 2008/2009
FIRST YEAR, SECOND SEMESTER (Jun./Sept., 2015)
EXTCS 106 – COMPUTER ORGANIZATION AND ARCHITECTURE

Answer all questions

Time allowed: 02 hours

- a) Briefly explain the following terms:
- i. *Computer Architecture*;
 - ii. *Computer Organization*.
- b) State what are the major structural components of CPU.
- c) Explain the functional view of a computer with the aid of diagrams.
- d) Convert the following octal numbers to binary numbers:
- i. 457;
 - ii. 72.
- e) Convert the following hexadecimal numbers to decimal numbers:
- i. 83FA;
 - ii. 12B.
- a) Explain the Von- Neumann architecture.
- b) Briefly describe the basic instruction cycle with the aid of diagrams.
- c) State and Prove the *De Morgan's* laws.
- d) Draw a circuit diagram corresponding to the following Boolean expressions:
- i. $(AB + C) D$;
 - ii. $\overline{AB} + \overline{(B+C)}$.

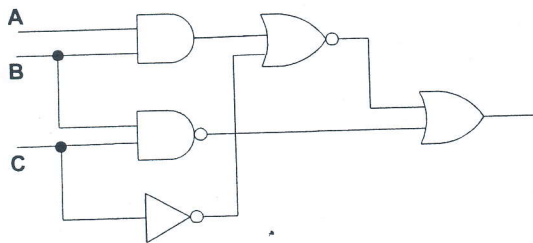e) Show the behavior of the following circuit with a truth table:




03.

- What are the three common ways of representing signed numbers?
- Briefly explain the function of a half adder.
- Draw the logic circuit for a half adder and write down the Boolean expression with respect to the circuit.
- Draw the logic circuit for a full adder using two half adders.
- Perform the following calculations in binary using 8 bit two's complement representation:

- $12 + (-69)$;
- $(+8) - (+5)$.

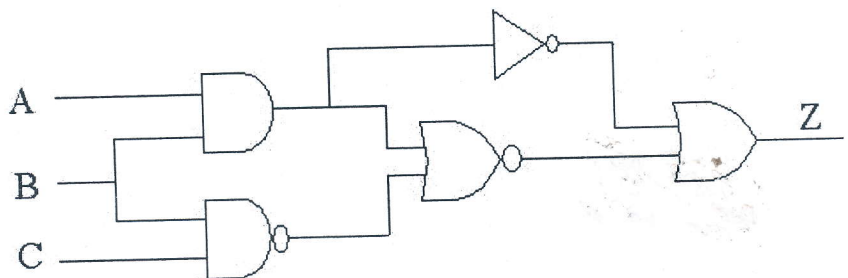04.

- What is meant by "**K-Map**" (Karnaugh Map)?
- Briefly explain the advantages of K-Map.
- Consider the following combinational logic circuit:



- Derive the truth table and draw a K-Map for the above circuit.
- Derive a reduced Boolean expression for the output Z.