

EASTERN UNIVERSITY, SRI LANKA

FIRST EXAMINATION IN SCIENCE - 2002/2003

SECOND SEMESTER

(MARCH/APRIL 2004)

REPEAT


PH 104 AC THEORY

Time: 01 hour.

Answer ALL Questions

---

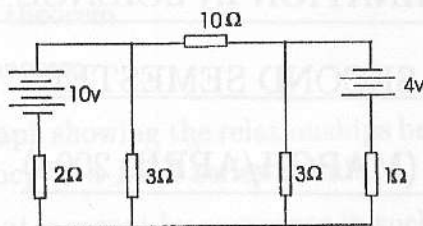1. State Thevenin's and Norton's theorems and illustrate one of them with an example.



Find the current in the  $10\Omega$  resistor of the above circuit using

- (i) Thevenin's theorem
  - (ii) Norton's theorem
2. (a) Sketch a graph showing the relationships between current, impedance and frequency in a  $LCR$  series circuit.
- (b) Explain what is meant by resonance in such a circuit and calculate the frequency at which it occurs in terms of  $L$  and  $C$ .
- (c) A series circuit with  $R = 5\Omega$ ,  $C = 20\mu F$  and a variable inductance  $L$  has an applied voltage  $V = 10 \text{ Volts}$  with a frequency of  $1000 \text{ radsec}^{-1}$ .  $L$  is adjusted until the voltage across the resistor is a minimum. Find
- (i) inductance of the inductor
  - (ii) the current through the circuit
  - (iii) the voltage across the capacitor
  - (iv) the voltage across the resistor