

EASTERN UNIVERSITY, SRI LANKA

FIRST EXAMINATION IN SCIENCE - 2002/2003

SECOND SEMESTER


(MARCH/APRIL 2004)

PH 104 AC THEORY

Time: 01 hour.

Answer ALL Questions

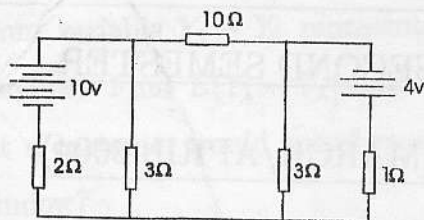1. State Thevenin's and Norton's theorems and illustrate one of them with an example.



Find the current in the 10Ω resistor of the above circuit using

- (i) Thevenin's theorem
 - (ii) Norton's theorem
2. (a) Sketch a graph showing the relationships between current, impedance and frequency in a LCR series circuit.
- (b) Explain what is meant by resonance in such a circuit and calculate the frequency at which it occurs in terms of L and C .
- (c) A series circuit with $R = 5\Omega$, $C = 20\mu F$ and a variable inductance L has an applied voltage $V = 10 \text{ Volts}$ with a frequency of 1000radsec^{-1} . L is adjusted until the voltage across the resistor is a minimum. Find
- (i) inductance of the inductor
 - (ii) the current through the circuit
 - (iii) the voltage across the capacitor
 - (iv) the voltage across the resistor