

EASTERN UNIVERSITY, SRI LANKA

THIRD EXAMINATION IN SCIENCE - 2001/2002

(APRIL 2002)

PH 301 ELECTRONICS II


Time: 01 hour.

Answer ALL Questions

---

1. What is meant by feed back in an electronic circuit. Discuss the advantages of the negative feedback. Derive the expression for closed loop gain  $A$  in terms of feed back fraction  $\beta$  and open loop gain  $A_0$ . For the following series-parallel feed back amplifier calculate

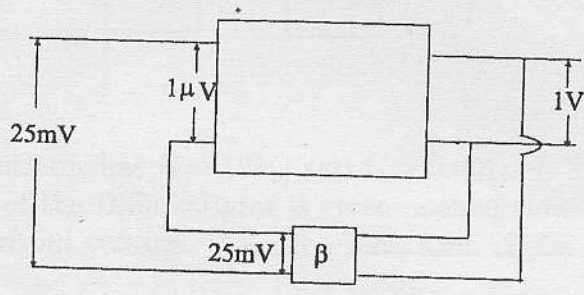
- (i) open-loop gain
- (ii) gain of feed back loop
- (iii) closed-loop gain



2. Briefly explain the characteristics of an ideal Operational Amplifier. Find the output voltage in terms of input voltage of the following Operational Amplifier.

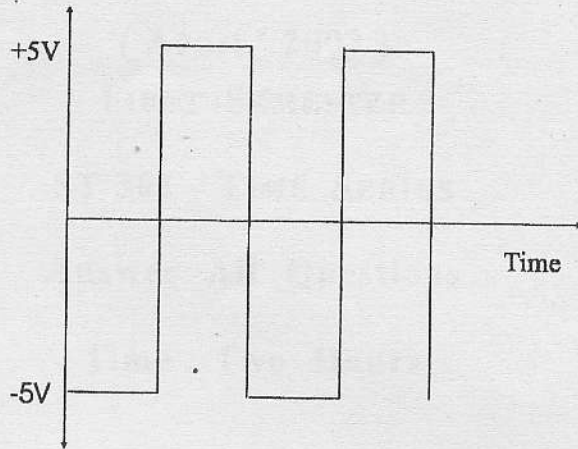- (i) Inverting
- (ii) Integrator
- (iii) Differentiator

An Integrator has  $R = 10\text{k}\Omega$  and  $C = 0.1\mu\text{F}$ . Its input is a  $1\text{kHz}$  square wave of  $5\text{volts}$  amplitude as shown in the figure. Determine the output voltage of the Integrator. Draw the wave form of the output.



A Differentiator has  $R = 10k\Omega$  and  $C = 0.001\mu F$ . The input voltage wave form of the Differentiator is given in the following figure. Determine the output voltage. Draw the wave form of the output.

