

EASTERN UNIVERSITY, SRI LANKA

SECOND EXAMINATION IN SCIENCE - 2004/2005

FIRST SEMESTER - JANUARY/FEBRUARY 2006

PH 202 - ELECTRONICS I


Answer ALL questions.

Time: One hour

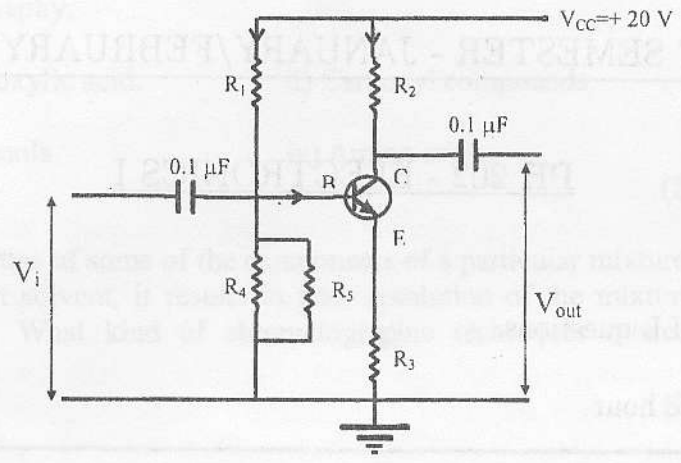Q1. Describe the action of a bipolar junction transistor.

Sketch and explain the input and output characteristics curves of a transistor.

A silicon transistor is used in the self biasing arrangement as shown in the diagram below with $V_{CC} = +20V$, $V_{BE} = 0.7 V$, $R_1 = 80 k\Omega$, $R_2 = 20 k\Omega$, $R_3 = 50 k\Omega$, $R_4 = 20 k\Omega$, $R_5 = 60 k\Omega$ and $\beta = 100$. Compute the collector current I_C .



Now a transistor is substituted with $\beta = 150$ into the circuit. Find the percentage change in I_C .

Q2. By explaining the meaning of intrinsic semiconductors discuss how an intrinsic semiconductor, for example pure silicon, may be converted into

- (a) an N-type semiconductor
- (b) a P type semiconductor and

briefly explain the mechanism of electrical conduction in the above two cases.

A narrow germanium bar having a circular cross section area measuring 1 mm diameter is doped with phosphorus of a concentration 10^{20} cm^{-3} . If the mobility of the electron in germanium is $3600 \text{ cm}^2\text{V}^{-1}\text{s}^{-1}$ and $e = 1.6 \times 10^{-19} \text{ C}$, calculate

- (a) the resistivity of the doped semiconductor, and
- (b) the length of the bar to provide a total resistance of 5 kΩ.