

EASTERN UNIVERSITY, SRI LANKA

THIRD EXAMINATION IN SCIENCE 2005/2006 (AUG-SEP. 2007)

FIRST SEMESTER

PH 301 – ELECTRONICS II


Time: 01 hour.

Answer ALL Questions.



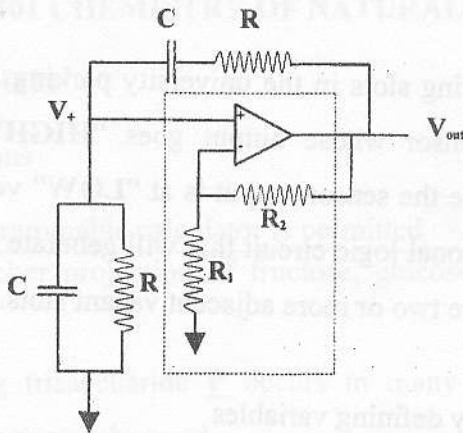1. Explain what is meant by positive and negative feedback as applied to electronic circuits.

A Wien Bridge Oscillator Circuit is shown in the figure below. The Oscillator consists of a non-inverting amplifier and an RC feedback network.



- (i) Show that the transfer function for the RC feedback network outside the

broken rectangle is
$$\frac{v_+}{v_{out}} = \frac{1}{3 + j\left(\omega RC - \frac{1}{\omega RC}\right)}$$

- (ii) If $R=10\text{k}\Omega$ and $C=10\text{nF}$, at what frequency will the circuit oscillate?

Hence evaluate $\frac{v_+}{v_{out}}$ at this frequency.

- (iii) Show that the gain of the ideal non-inverting amplifier inside the broken

rectangle is given by
$$\frac{v_{out}}{v_+} = \frac{R_1 + R_2}{R_1}$$

- (iv) Hence calculate the value of R_2 needed to promote oscillation when $R_1=10\text{k}\Omega$.

- (v) The circuit would probably not start oscillation when switched on or, alternatively, may produce a clipped waveform. Why does this happen?

How could you modify the circuit to prevent this from happening?

2. Draw the symbols and truth table for the following.

- (a) AND
- (b) OR
- (c) NAND
- (d) NOR

There are four adjacent parking slots in the university parking area. Each slot is equipped with a special sensor whose output goes "HIGH" when a car is occupying the slot. Otherwise the sensor output is at "LOW" voltage. You are to design and draw a combinational logic circuit that will generate a "HIGH" output voltage if and only if there are two or more adjacent vacant slots.

- (a) Formulate the problem by defining variables
- (b) Write the truth table for the problem
- (c) Convert the truth table into logical expression
- (d) Simplified the logical expression
- (e) Draw the simplified logic circuit using basic logic gates.