

EASTERN UNIVERSITY, SRI LANKA
FIRST EXAMINATION IN SCIENCE 2002/2003 (EXTERNAL DEGREE)
(SECOND SEMESTER)

EXTPH 104 AC THEORY

Time : 1 Hour

Answer All Questions

1. (a). Write down expressions for capacitive and inductive reactance
- (i) 0.3 H inductor has a resistance 6000Ω when connected to an AC power supply. What is the frequency of the supply?
 - (ii) A capacitor with capacitance $0.1 \mu\text{F}$ is connected to 100 V, 50 Hz supply. Calculate the reactance of the capacitor and the current flowing through the capacitor.
- (b). 50Ω resistor is connected in series with a $1 \mu\text{F}$ capacitor and this combination is connected to a 200 V, 1000 Hz supply. Calculate
- (i) the circuit impedance
 - (ii) the circuit current
 - (iii) the phase angle
 - (iv) the voltages across the capacitor and the resistor.
2. A resistor with resistance R, a capacitor with capacitance C and an inductor with inductance L are connected in series to a power supply of voltage V and frequency f. Determine
- (i) the circuit impedance
 - (ii) the phase angle

When the circuit is at resonance determine the above values and the resonant frequency. Determine the voltages across C and L at resonance.

If $R = 100 \Omega$, $C = 0.1 \mu\text{F}$, $L = 0.01 \text{ H}$ and $V = 100 \text{ V}$ calculate

- (i) Resonant frequency
- (ii) Circuit current at resonance
- (iii) Q - factor of the circuit.