

PERMANENT REFERENCE

0014000416  
HRA

## CONSTRUCTION OF ALU DEMONSTRATION BOARD.



BY

MAALATHY SOORIYAKANTHAN.

PROCESSED  
Main Library, EUSL



FACULTY OF SCIENCE,  
EASTERN UNIVERSITY, SRILANKA.  
SEPTEMBER 1999.

## Abstract.

The arithmetic logic unit (ALU) is the ‘heart’ of all microprocessors and computers. The role of the ALU, which lies at the center of every computers; can be simply understood using an ALU demonstration board.

A 4-bit and a 8-bit ALU demonstration boards, completely based on binary system, are constructed. Each performs a total of 48 functions, which include 32 arithmetic and 16 logic functions.

## **CONTENTS.**

---

<b>Acknowledgments</b>	v
<b>Abstract</b>	vi
<b>List of abbreviations</b>	vii
<b>CHAPTER 1</b>	
<b>Introduction</b>	1
<b>CHAPTER 2</b>	
<b>Background Theory</b>	3
<b>    2.1. Introduction</b>	3
2.1.1. Number system	4
2.1.2. Binary arithmetics	5
2.1.2.1. Addition	5
2.1.2.2. Subtraction	5
2.1.2.3. Multiplication	6
2.1.2.4. Computer multiplication	7
2.1.2.5. Division	7
2.1.2.6. Computer division	8
<b>    2.2. Logic and Boolean Algebra</b>	9
2.2.1. Logic	9
2.2.2. Gates and truth tables	9
2.2.3. Laws of Boolean algebra	10
2.2.4. Inverted output logic	11
2.2.4.1. Simple combination of gates	12
2.2.5. Integrated circuits	13
2.2.5.1. Digital electronics	13
2.2.5.2. Digital logic families	13
2.2.5.3. Properties of TTL and CMOS	14
2.2.5.4. Some uses	14
2.2.5.5. Logic gates	15
2.2.5.6. Pin connections	15
<b>    2.3. Combinational Logic</b>	17
2.3.1. Multiplexers and Demultiplexers	17
2.3.2. Arithmetic Circuitry	17
2.3.3. Magnitude Comparators	22

<b>2.4. Sequential Logic</b>	23
<b>2.4.1. Flip-Flops</b>	23
2.4.1.1. JK Flip-flop	24
2.4.1.2. Master-Slave and edge-triggered flip-flop	24
<b>2.4.2. Counters</b>	25
2.4.2.1. Ripple counter	25
2.4.2.2. Modulo counter	26
2.4.2.3. Up-down counters	26
<b>2.5 Analogue Circuits</b>	27
2.5.1. Rectifier	27
2.5.2. Mechanism of light emission	27
2.5.3. Transistor as a switch	28
<b>CHAPTER 3</b>	
<b>Instrumentation</b>	29
<b>3.1. Introduction</b>	29
<b>3.2. Description of the main components</b>	30
3.2.1. 74LS181 (ALU)	30
3.2.2. 74LS182 (carry-look-ahead generator)	30
3.2.3. 74LS93 (binary counter)	30
3.2.4. 555 (timer)	31
3.2.5. 74LS244 (buffer)	31
3.2.6. 74LS154 (demultiplexer)	31
3.2.7. 74LS85 (comparator)	31
3.2.8. Power supply	32
3.2.9. Light-emitting diode	32
3.2.10. Mechanical switches	33
<b>3.3. Description of the design</b>	35
<b>3.4. Construction</b>	38
<b>3.5. Examples</b>	40
3.5.1. Few examples of logic and arithmetic operations for 4-bit	40
3.5.2. Few examples of logic and arithmetic operations for 8-bit	42

<b>CHAPTER 4</b>	
<b>Discussion</b>	44
<b>References</b>	47
<b>Appendix A: Function table</b>	48
<b>Appendix B: List of parts</b>	49
<b>Appendix C: Internal diagram &amp; Pin connection of ICs</b>	51